

## Fire Alarm

### Hardware Requirements :

- 1) Flame sensor (Analogue Output) - (1)
- 2) Arduino - (1)
- 3) Bread board - (1)
- 4) LED- (2)
- 5) Buzzer - (1)
- 6) Connecting wires - (as per need)

### Connection :

Flame sensor to Arduino :

vcc -> vcc

gnd -> gnd

A0 -> A0

### **Led interfacing to Arduino**


**LED +ve** is connected to **9th pin** of Arduino

**LED -ve** is connected to **gnd pin** of arduino **Buzzer interfacing to Arduino**

**Buzzer +ve** is connected to **12th pin** of Arduino

**Buzzer -ve** is connected to **GND** pin of Arduino

## **Result :**

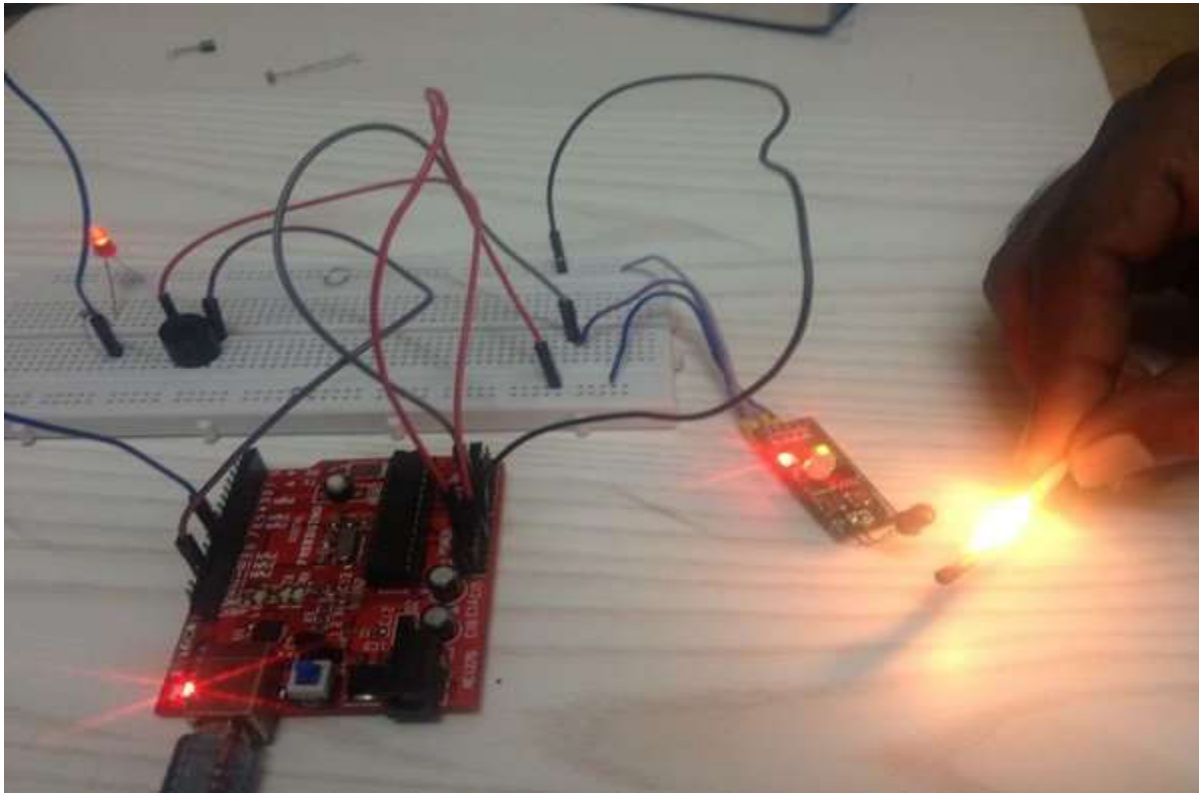

As we will bring flame near to flame sensor, the buzzer will buzz on and u will be warned for the flame detection.